


VHDL: V Hardware Description Language

VHSIC: Very High Speed Integrated Circuit

Two main statements: Entity & Architecture

Entity	Declares ports (interface to outside world)
--------	---


Architecture	Describes connections inside the entity
--------------	---

 

entity first_circuit is

```
port ( A:      in      std_logic;
       B:      in      std_logic_vector(3 downto 0);
       C:      in      std_logic;
       X:      out     std_logic_vector(6 downto 0);
       Y:      out     std_logic;
       Z:      out     std_logic ) ;
```

end entity ;

 

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity half_adder is
```

```
port(
```

```
    x,y: in std_logic;
```

```
    sum, carry: out std_logic);
```

```
end entity;
```


```
architecture myadd of half_adder is
```

```
begin
```

```
    sum <= x xor y;
```

```
    carry <= x and y;
```

```
End architecture;
```

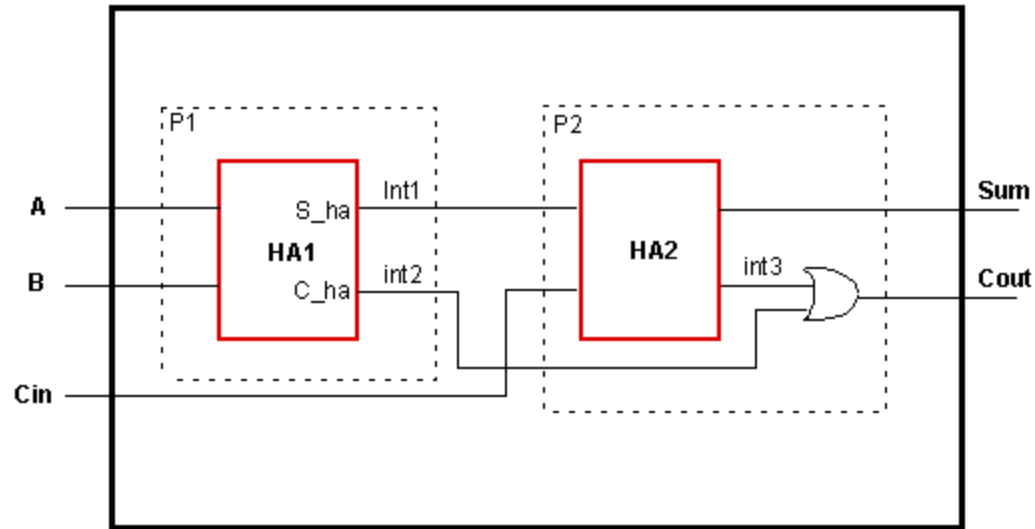

- Int1, Int2, and Int3 are declared as SIGNAL

architecture main of full_adder is

Signal Int1, Int3: std_logic ;


Signal Int2: std_logic: '1' ;

begin

...

End architecture;

 - Inside the body of the architecture, all statements run concurrently.



```

1  ARCHITECTURE MAIN OF MY_ENTITY IS
2  SIGNAL K, L, M : std_logic ;
3  BEGIN
4      K = A and B ;
5      L = K or C ;
6      M = not D ;
7      Output = L nand M ;
8  END MAIN ;
9
10
11
12  ARCHITECTURE MAIN OF MY_ENTITY IS
13  SIGNAL K, L, M : std_logic ;
14  BEGIN
15      Output = L nand M ;
16      L = K or C ;
17      K = A and B ;
18      M = not D ;
19  END MAIN ;
20
21
22

```